

Structuring a SMPS Course, Part II: Laboratory

THUAS Delft, The Netherlands

Prof oP. dr.ir. P.J. van Duijsen(presenter), ing D.C. Zuidervliet



www.dc-lab.org

Mai 26th 2022

- ① Introduction:
- ② Laboratory Exercise Outline
- ③ Laboratory Exercise Topics
- ④ Laboratory Exercise Methods
- ⑤ Laboratory Exercise Objectives
- ⑥ Conclusions


Switched Mode Power Supply Laboratory


What to teach?

- Basic converter topology(Buck, Boost,.....)
- Components(Inductor, Capacitor, Mosfet, Diode)
- Control(Voltage Mode, Peak Current Mode, Constant on time,...)
- Measurements(Learn how to measure)


Boost converter

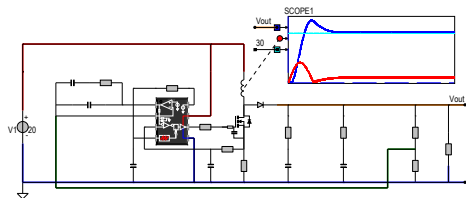- Topology
 - Most important components
- Components
 - Basic design
- Control
 - Dedicated IC
- Measurements
 - Detailed Current shape measurement



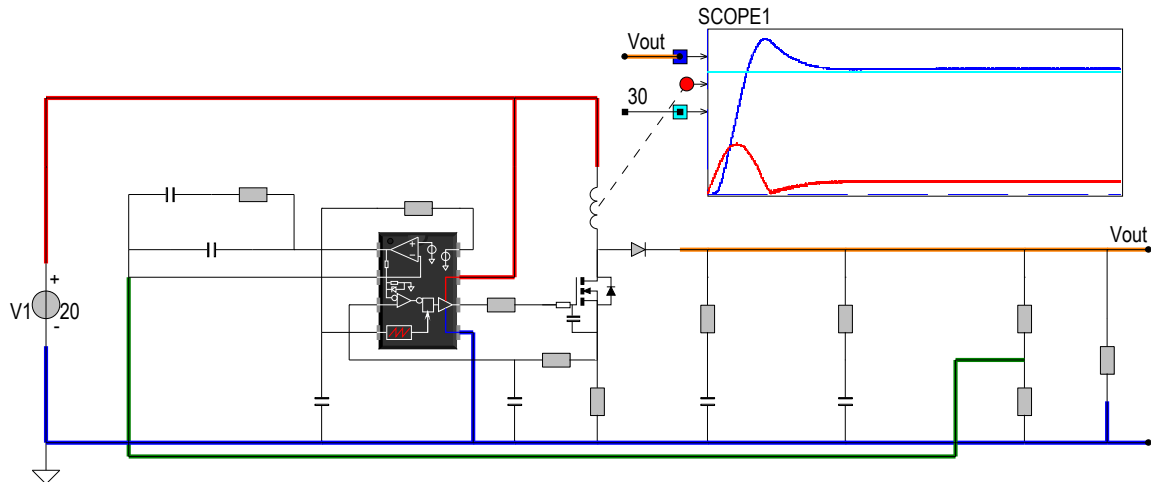


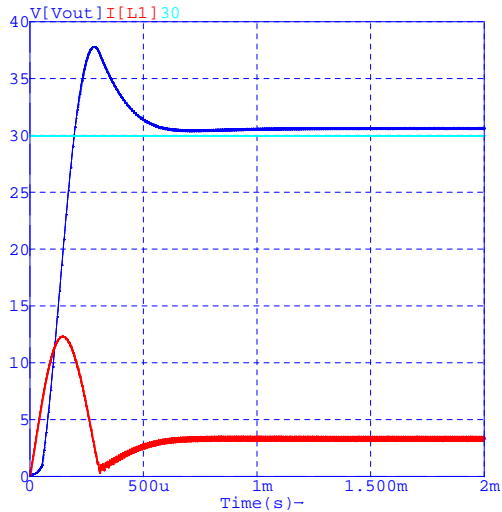
Figuur: Boost converter simulation in Caspoc. Peak current mode control using the uc3842.




Boost converter simulation results. Output voltage(blue) and inductor current(red).

Lecture	Week	Topic	Lecture objective	Laboratory objective
1	1	Basic converters	Switching Cell	Build pwm generator
2	2-3	Operation Principles	Input-output relations and inductor ripple current calculation	Building a breadboard boost converter
3	4	Waveforms	Voltage and current waveforms for continuous and discontinuous mode	Debugging and performing measurements on the breadboard converter
4	5-6	Components	Sizing all main components for storage and filtering	Assembling a Boost converter on PCB(SMD or Through Hole)
5	7	Constraints	Understanding the datasheet parameters for mosfet and magnetic cores	Measuring the real waveforms on the constructed PCB
6	1-2	Magnetic	Design of magnetic components	Winding and testing a self made inductor
7	3-4-5	Layout Thermal and	Origin of Electromagnetic conducted and radiated interference, Efficiency and loss calculation	PCB design and EMI, measuring the losses and heating of the inductor and Mosfet
8	6-7	Control	Closed loop control	Measuring converter stability

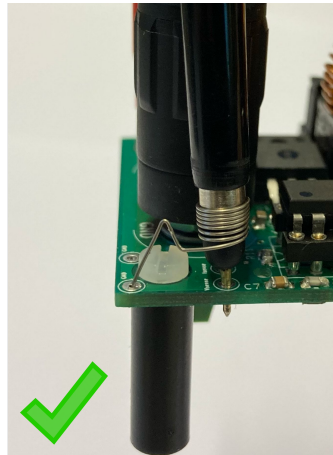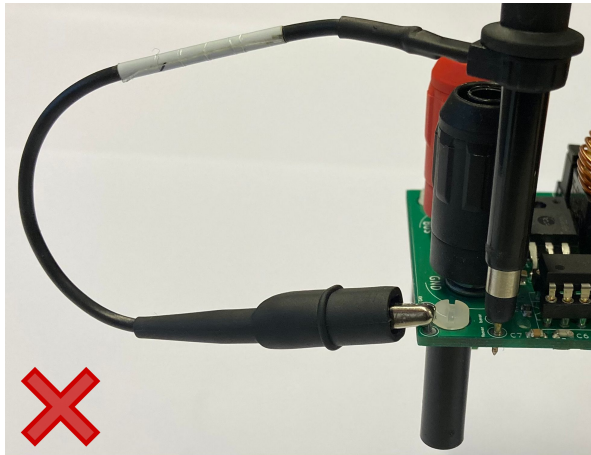
Tabel: Lecture and week number with topic and lecture and laboratory objectives.



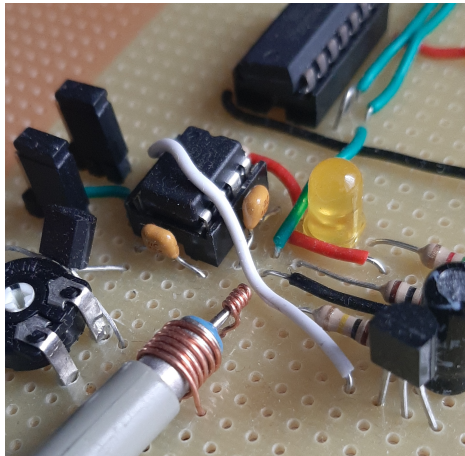A long ground wire of the probe may give false signals on the oscilloscope. Proper connection using a pig tail reduces ground loops and give better measurements.



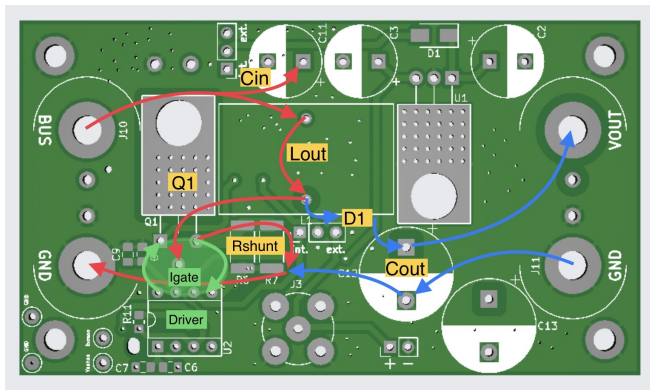
Low cost pigtail soldered on a perfboard for measuring the oscillator frequency signal on a UC3842 control IC.




Boost converter using SMD components on printed circuit board. The layout is optimized and the loop area is minimized. Current paths during continuous mode. During T_{on} the current flows through the inductor, Mosfet and sense-resistors, see the red arrows. During the freewheeling period T_{off} , the current stored in the inductor, flows via the diode over the output capacitors to the output, see the blue arrows.

Methods

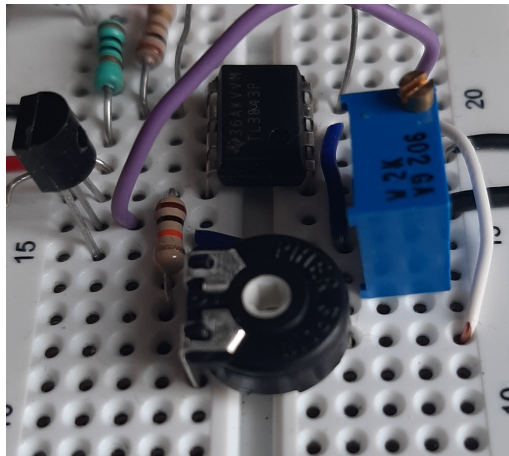- Breadboard
- Hardware trainer
- Assembled PCB




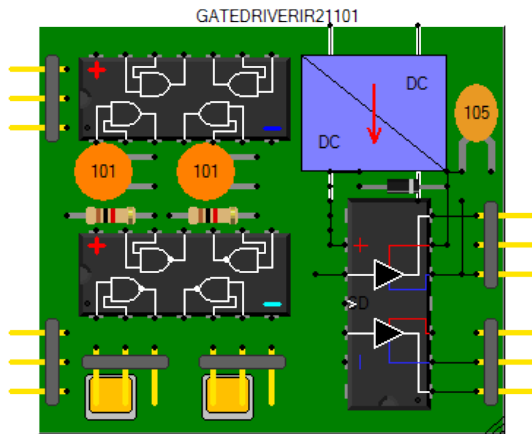Single uc3842 power management IC to create pulse width modulator with variable frequency and duty cycle, to demonstrate and experiment with a general current mode control IC.




Gatedriver circuit board, that can be interchanged to study the impact of various gate driver ICs on the U2L board.


Boost assembled on breadboard

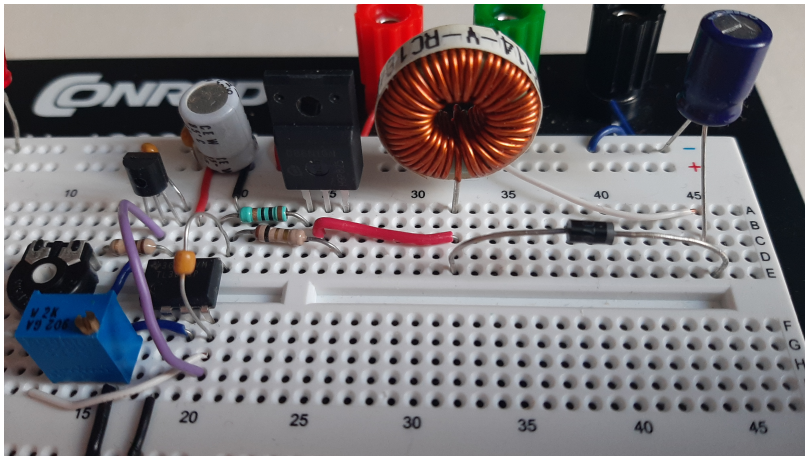

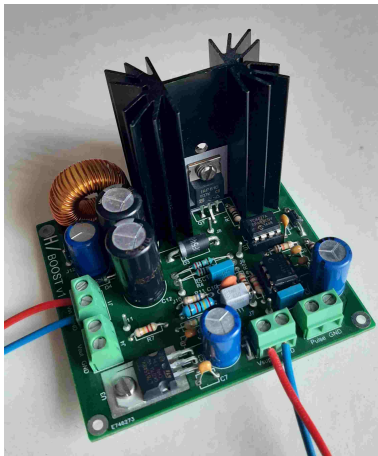Low cost set up of a boost converter with limited power capabilities, but allowing to demonstrate the basic waveforms and principles.




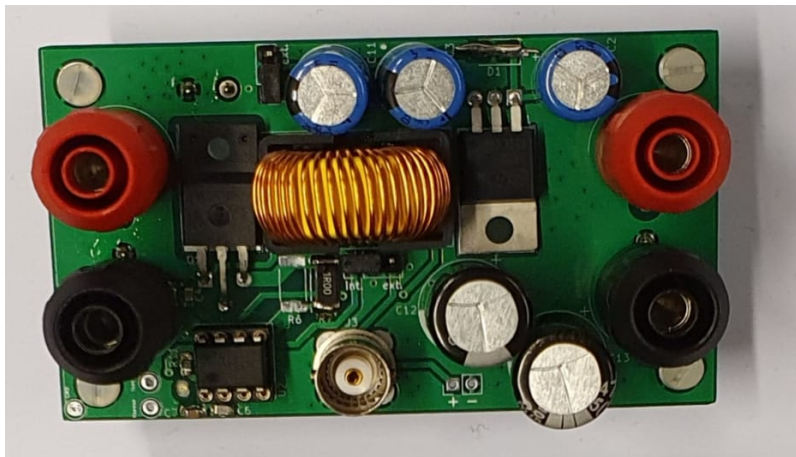Fully assembled boost converter on a through hole PCB.




Fully assembled boost converter on an optimized PCB using SMD components.

Measurements PCB through-hole

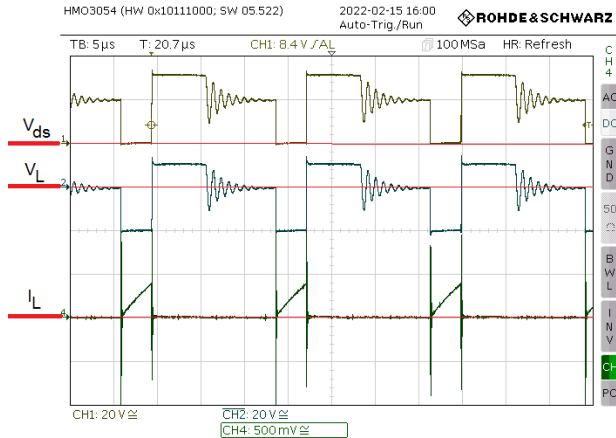

Through Hole Boost converter measurement. From top to bottom, V_{ds} , V_L , V_{Rsense}

Measurements PCB using SMD components

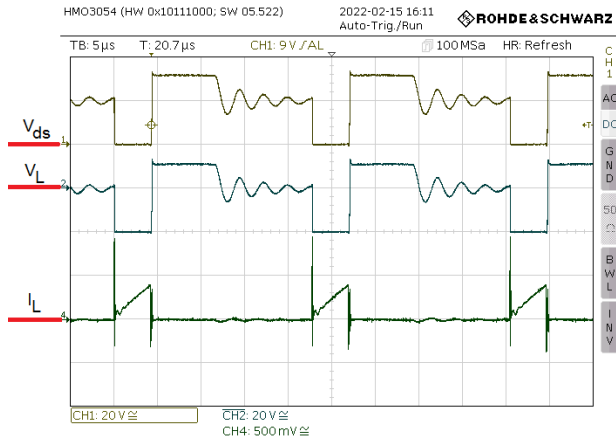

SMD Boost converter measurement. From top to bottom, V_{ds} , V_L , $V_{R_{sense}}$

*Basic objectives***B** PWM

Build a basic pulse width generator using an industry standard power management IC.

M Converter

Extend the pulse width generator with a Boost converter on a breadboard, to understand the switching cell principle. Use a constant duty cycle only. Measure input and output voltage and current waveforms, as well as the inductor current.

B Assembling

Assemble a Boost converter on PCB either Through Hole or SMD.

D Component ratings

Measure all voltage and current waveforms and compare for various design methods (Breadboard, Through Hole PCB or SMD PCB). Verify component ratings, for example maximum V_{DS} for the Mosfet, or maximum current through the Mosfet, inductor and diode.

M PCB design

Understand the difference in PCB design and measure the conductive EMI by measuring the ringing on the Mosfet. Add a second output capacitor and observe the reduction of the output voltage ripple.

Tabel: Basic Objectives(B:Build, D:Design, M:Measure)

*Extended objectives***D** Magnetic design and switching frequency

Design a custom inductor using ferrite cores and make a trade-off between losses and size.

D Thermal design

Losses and heat sink design. Calculate the thermal resistors in the thermal path from the Mosfet into the heat sink. Design the size of the heat sink and estimate the losses losses and final semiconductor temperature.


M Control

Measure the bandwidth of the control and by changing components in the control feedback loop, see the functioning and influence of each component in the control. For example, adding slope compensation, by adding a single resistor to avoid subharmonic oscillations. Increase output capacitor ESR to reduce overshoot during load changes. Load the boost converter with a variable pulsating load and observe the bandwidth of the control loop.

Tabel: Extended Objectives(D:Design, M:Measure)

- Course outline
- Topics that should be included
- Methods (Breadboard, Hardware Trainer, PCB)
- Objectives (Basic and Extended)

Thank you!
www.dc-lab.org

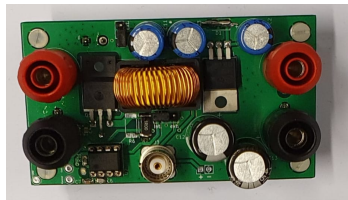

Thanks to Christian Nagy, Koen de Bruin and Holly Engelbrecht for designing and constructing the SMD-PCB board.